

# Introduction to Verilog

*KAIST, School of EE*

Computer Architecture and Memory systems Laboratory

**KAIST EE**

***CAMELab***



# Outline

---

- **Lab Class Operating Plan**
- **Verilog HDL: Introduction**
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- **Verilog Simulation**
  - Verilog RTL Simulation
  - Simulation using Modelsim

# Outline

---

- **Lab Class Operating Plan**
- Verilog HDL: Introduction
- Verilog Syntax
- Verilog Simulation

# Basic Direction

---

- **Lab Class**

- Dealing with practical implementation of what you have learned in the class

- **Lab Assignment**

- Verilog implementation of what you learned in lab class
  - Verilog: A programming language for hardware design

# QnA on Class and Assignment

---

- **Send an e-mail to TAs**
  - Note that we have designated TA for each lab assignment
- **Use Office Hours of TAs**
  - Refer to the notice on KLMS

# Outline


---

- Lab Class Operation Plan
- **Verilog HDL: Introduction**
- Verilog Syntax
- Verilog Simulation
 
# Introduction to Verilog

- **What is Verilog HDL?**

- Hardware Description Language (HDL) for hardware (ASIC or FPGA) design/simulation/verification
- Similar to C language
- Providing a range of abstractions
- RTL: Register Transfer Level
  - Abstract hardware model described in Verilog



Example HDLs: Verilog, VHDL..  
In this lab, **Verilog** is used!

# Differences from Software

---

- Software is inherently sequential
  - Operation executed in sequential order
- Hardware blocks run in parallel (at the same time)
  - Use event-driven paradigm
  - HDL provide constructs for both parallel & sequential oper.

**Software**  
*execute sequential*

```
ret1 = x + y;  
ret2 = x - y;
```



**Hardware**  
*2 gates work at the same time*

```
ret1 = a & b;  
ret2 = a | b;
```



# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps

module AND (
    input    [3:0] A,
    input    [3:0] B,
    output   [3:0] Q);

    reg [3:0] Q;

    always begin
        Q = A & B;
    end
endmodule
```

*Starting from here.  
(In case of designing  
Multi-bit AND chip)*

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps
```

← 1ns: the min. unit of delay  
100ps: the min. unit of simulation

```
module AND (  
    input    [3:0] A,  
    input    [3:0] B,  
    output   [3:0] Q);
```

```
    reg [3:0] Q;
```

```
    always begin  
        Q = A & B;
```

```
    end  
endmodule
```

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps
```

```
module AND (
```

← Module start

```
    input      [3:0] A,
```

```
    input      [3:0] B,
```

```
    output     [3:0] Q);
```

```
    reg [3:0] Q;
```

```
    always begin
```

```
        Q = A & B;
```

```
    end
```

```
endmodule
```

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps
```

```
module AND (
```

```
    input    [3:0] A,
```

```
    input    [3:0] B,
```

```
    output   [3:0] Q);
```

← I/O **ports** declaration

```
    reg [3:0] Q;
```

```
    always begin
```

```
        Q = A & B;
```

```
    end
```

```
endmodule
```

# Verilog Example


- Simple AND Module

```
`timescale 1ns / 100ps

module AND (
  input  [3:0] A,
  input  [3:0] B,
  output [3:0] Q);

  reg [3:0] Q;

   always begin
    Q = A & B;
  end
endmodule
```



← Declaration of Output Q  
as a register

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps

module AND (
    input    [3:0] A,
    input    [3:0] B,
    output   [3:0] Q);

    reg [3:0] Q;

    always begin
        Q = A & B;
    end
endmodule
```

← If there are any change of values in a block (from **begin** to **end**, like { } in C language), the statement  $Q = A \& B$  is always executed.

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps

module AND (
    input    [3:0] A,
    input    [3:0] B,
    output   [3:0] Q);

    reg [3:0] Q;

    always begin
        Q = A & B;
    end
endmodule
```

← Assign A&B in the register Q

# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps

module AND (
    input    [3:0] A,
    input    [3:0] B,
    output   [3:0] Q);

    reg [3:0] Q;

    always begin
        Q = A & B;
    end
endmodule
```

← 'AND' Module ends here.



# Verilog Example

- Simple AND Module

```
`timescale 1ns / 100ps

module AND (A, B, Q);
    input    [3:0] A;
    input    [3:0] B;
    output reg [3:0] Q;

    always begin
        Q = A & B;
    end
endmodule
```

← Looks different, but functionally equivalent to the codes shown in previous slide

# Timescale

---

``timescale 1ns / 100ps`

- **Declaration of Time Units for Simulation**

- Generally inserted at the beginning of the code
  - ``timescale <Delay Unit> / <Simulation Unit>`

- **Delay Unit:** The min. time unit of Delay cmd.

#100;     // Delay for 100 \* 1 ns

- **Simulation Unit:** The min. time unit of Sim.

- The timing resolution of simulation

# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- **Verilog Simulation**

# Module Concept in Verilog

- **Building Blocks** for Verilog Hardware Design
  - A chip itself or a component of a chip
  - Similar to “class” in programming languages
- **Interface + Behavior**
  - Interface: Input and Output (**Ports**)
  - Behavior: How does the module work?
  - How are the outputs generated w.r.t. the input?


*Port declaration*

```
module AND (input A, input B, output Q);  
    assign Q = A & B;  
endmodule
```

*Module Body*

# RTL Module Structure

- **Module Declaration**

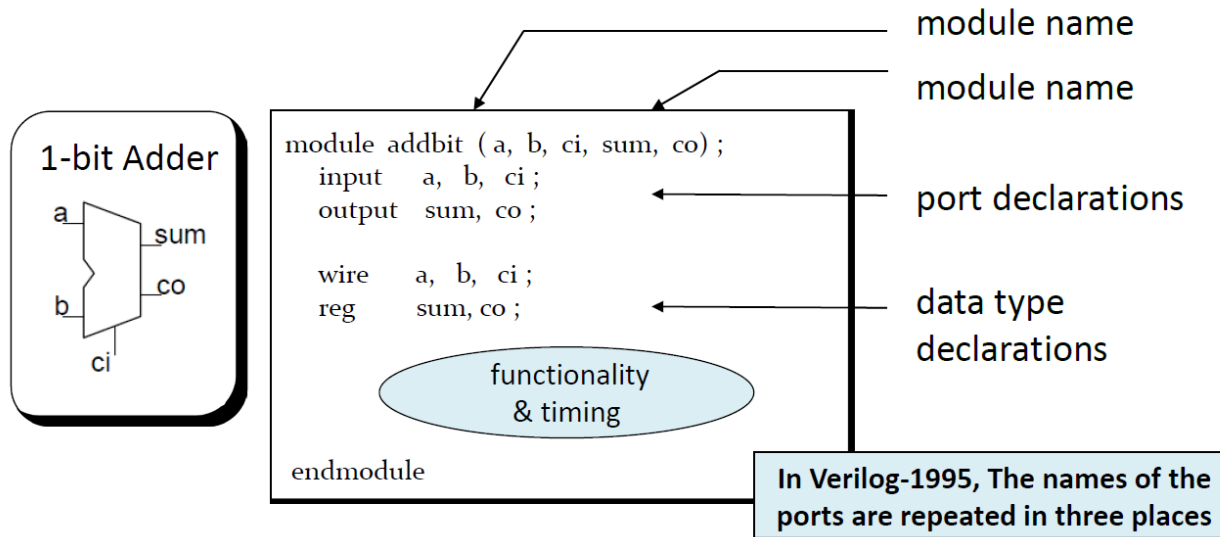

- Module **name**: a user-defined name for the model
- Module **ports**: signals coming in and going out
  - Port declaration: direction, bit width, wire/reg
- Data type: wire vs reg


# Module Instantiation

- **Instantiation:** Similar to a class call

```
module AND (input A, input B, output Q);  
    assign Q = A & B;  
endmodule
```

```
module AND_test ();  
    reg X, Y; wire W;  
    AND aaa (X, Y, W);  
endmodule
```

*Instantiation  
(Positional mapping)*

 


# Module Instantiation

- Another way of instantiating modules

```
module AND (input A, input B, output Q);  
    assign Q = A & B;  
endmodule
```

```
module AND_test ();  
    reg X, Y; wire W;  
    AND aaa (.A(X), .B(Y), .Q(W));  
endmodule
```

*Instantiation  
(Named mapping)*

 


# Testbench for Test Designed Module

- **Testbench**

- Test signal generation and output data recording with instantiation of the designed module
- Test signal (stimulus) generation as input to DUT

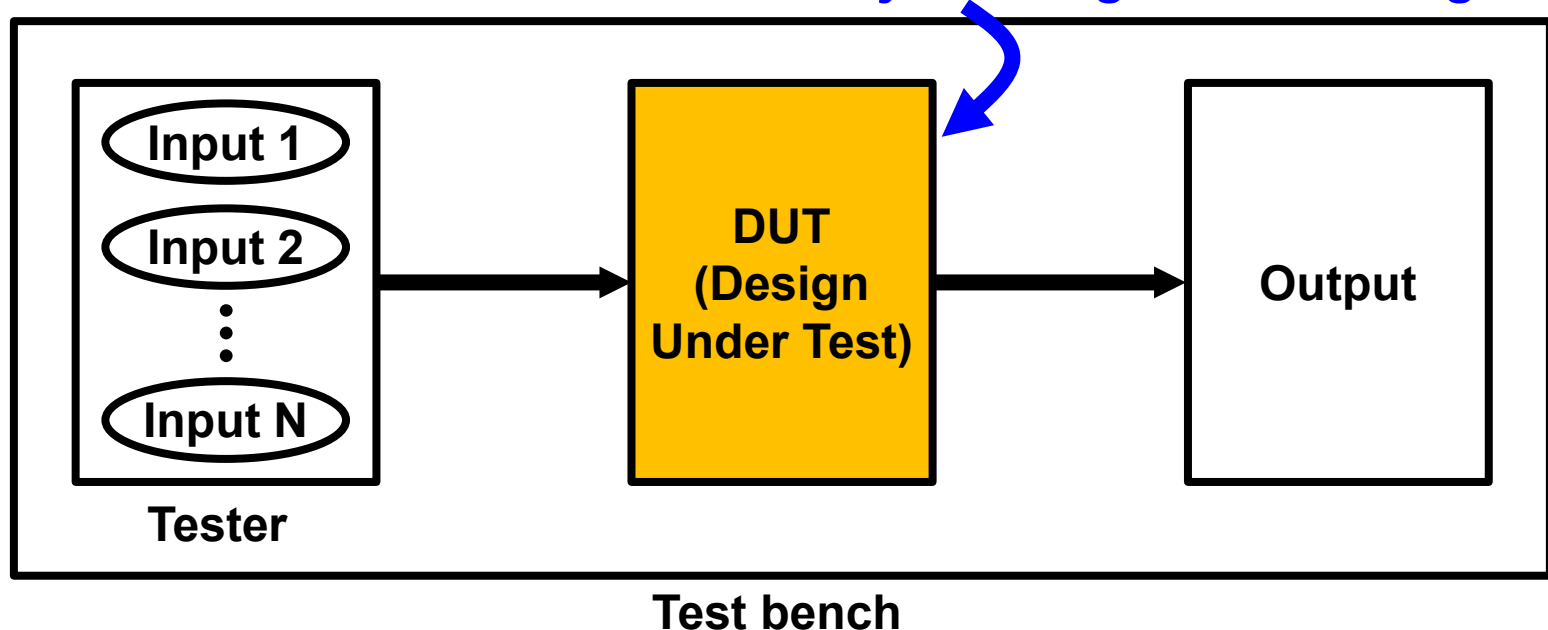*The Module Instantiation you designed in Verilog*





# Port Declaration

- **I/O of Module**

- Basically, regarded as **wire** (*input & output*)
- Optionally, can be also be declared as **reg** (*output*)
- **wire-wire** or **reg-wire** connection → *possible*
- **reg-reg** connection → *impossible*

```
module always_one (output Q);  
  reg Q; Declaring output Q as reg  
  initial Q = 1;  
endmodule
```

# Data Type

- **wire**

- Literally a piece of **wire as physical connection**

- **reg**


- 1-bit **D-flip flop** (1-bit register), **data storage element**

- **Bit Vector**

- ex) wire [0:31] addr; // Big-endian
- ex) reg [31:0] eax; // Little-endian (recommended)

- **Reference & Concatenation**

 - ex) addr // Entire addr bit vector  
addr[0] // 0<sup>th</sup> bit of addr  
addr[3:0] // 3<sup>rd</sup> ~ 0<sup>th</sup> bits of addr  
{eax[0], eax[31:1]} // eax's 0<sup>th</sup> bit + eax 31<sup>st</sup> ~ 1<sup>st</sup> bits



# Verilog Modeling Concepts

- **Structural (Gate-level) Modeling**

- Description using logic primitives
- *and, or, nand, not* ... and so on

- **Dataflow Modeling**


- Only for combinational functions
- Using statement *assign*

- **Behavioral Modeling**

- Providing high-level abstract description like C
- Using statement *always*
- Beware of “synthesizability”

- ➔ Not all behavioral models are synthesizable

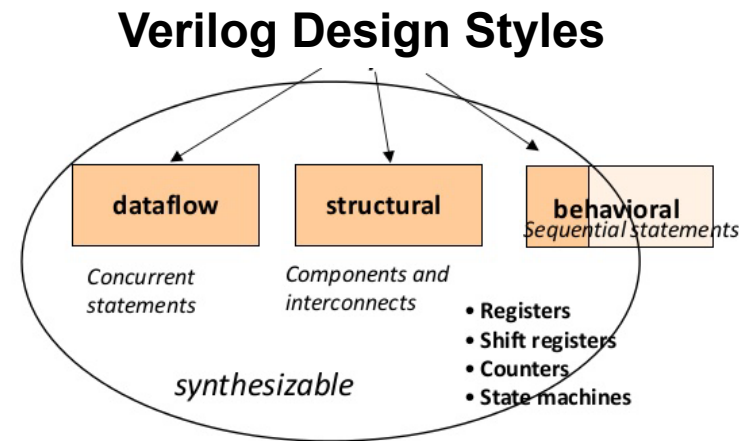- **RTL: Usually, Mix of Dataflow & Behavioral**




# Modeling Example

---



# Structural Modeling Example

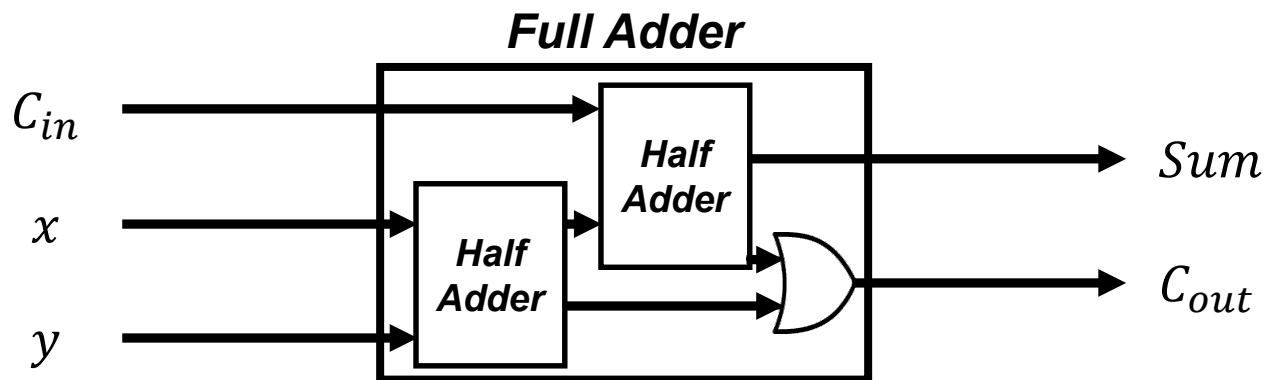

```
module Half_adder (x, y, sum, c_out);
  input      x, y;
  output     sum, c_out;

  xor (s,x,y);
  and (c,x,y);
endmodule
```



```
module Full_adder (x, y, c_in, sum, c_out);
  input      x, y, c_in;
  output     sum, c_out;
  wire      c1, s1, c2;

  Half_adder ha_1 (x, y, c1, s1);
  Half_adder ha_2 (c_in, s1, c2, sum);
  or(c_out, c1, c2);
endmodule
```

# Dataflow Modeling Example




```
module Full_adder (x, y, c_in, sum, c_out);  
  input    x, y, c_in;  
  output   sum, c_out;  
  
  assign {c_out, sum} = x + y + c_in;  
endmodule
```

# Behavioral Modeling Example



```
module Full_adder (x, y, c_in, sum, c_out);  
  input    x, y, c_in;  
  output   sum, c_out;  
  reg      sum, c_out; // need to be declared as reg type  
  
  always @ (x, y, c_in) begin // also @(*) or @(x or y or c_in)  
    {c_out, sum} = x + y + c_in;  
  end  
endmodule
```

# Sequential & Combinational Logic

 


## Guidelines:

- All module outputs should be registered
- Only use one clock per module

 
## • Combinational Logic

- *always @ (\*)* and blocking assignment (=)
- The output as a direct reflection of the input values
- Unable to use latching (registers)


 
## • Sequential Logic

- *always @ (posedge clk or negedge rst\_n)*
- Non-blocking assignment (<=)
- Latching: synchronized with clock → data storing





# Procedural Statements

- Procedural Statements as Code Block

```
module AND (input A, input B, output Q);  
  reg Q;  wire AnB;  
  assign AnB = A & B;  
  
  always begin  
    Q = AnB;  
  end  
endmodule
```

*Procedural Statement*

- Can be regarded as a code block like { } in C
- ***always*** and ***initial***

# Initial Procedure

---

- Initial Procedure at Testbench Initialization

<pre>initial begin   clk = 0;   x = 1; end</pre>	=	<pre>initial clk = 0; initial x = 1;</pre>
--	---	--

- Executed just once when module is instantiated
- Several statements can be contained b/w ***begin*** & ***end***
- Usually used when writing testbench to generate stimulus signals or to set initial values

# Always Procedure

- Always Procedure at Testbench Clock Gen.

```
reg clk;  
initial clk = 0;  
always begin  
    #50;  
    clk = ~clk;  
end
```

```
reg clk;  
initial clk = 0;  
always @(posedge clk) begin  
    #50;  
    a = ~a;  
end
```

- Always called when certain condition is satisfied
- Infinitely called when there is no condition
- Used in both **module design** and **testbench**
- Usually used when writing testbench **to generate clock signals**

# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - **Assignments**
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- **Verilog Simulation**

# Assignments

- Continuous and Procedural Assignments

```
module AND (input A, input B, output Q);  
  reg Q;  wire AnB;  
  assign AnB = A & B;  
  
  always begin  
    Q = AnB;  
  end  
endmodule
```

*Continuous Assignments*

*Procedural Assignments*

- Continuous: defining **wire** connections
- Procedural: allocating values at **registers**

# Continuous Assignments

- **Continuous Assignment for wire (assign)**

- Allocating connections b/w wires outside of procedure

```
wire a, b, c;  
assign c = a&b; // wire c is defined as a&b
```

- Can be used with declaration simultaneously

```
wire a, b;  
wire c = a&b;
```

- Not changed in the middle of simulation
- Used with delay for wire delay modeling

```
wire a, b, c;  
assign #10 c = a&b;  
// c is update to a&b after 10 delay unit
```

# Procedural Assignments

- **Procedural Assignment for Register (<=, =)**

```
reg clk;  
initial begin  
    clk = 0;  
end
```

- Storing values in reg
- Use with delay for delay modeling
  - ex) #10 clk = 0; *//assign 0 at clk after 10 delay*  
#10 clk = #20 tmp; *// read tmp after 20 delay*  
*// then store it in clk after 10 delay*
- Blocking (=) & Non-blocking (<=)

# Types of Procedural Assignments

- **Blocking Assignments**

```
reg a, b;  
initial begin  
    a = 0;  
    b = 1;  
end
```

*In the both codes,  
a=0 is executed first,  
and then b=1 is executed*

```
reg a, b;  
initial begin  
    a = 0;  
end  
Initial begin  
    b = 1;  
end
```

- Executed sequentially line by line (like C)
- Use “=” operator
- The order b/w procedures is also valid



# Types of Procedural Assignments

- Non-Blocking Assignments

```
reg a, b;  
initial begin  
    a <= 0;  
    b <= 1;  
end
```

*In the both codes,  
a<=0 and b<=1  
are executed  
simultaneously*

```
reg a, b;  
initial begin  
    a <= 0;  
    b <= 1;  
end
```

- Executed concurrently in parallel
- Use “<=” operator
- Does not matter with order

***DO NOT USE blocking (=) and non-blocking (<=)  
TOGETHER in the same procedure!***


# Blocking vs Non-blocking

- Data Flow w.r.t Time (Initialized as a=0, b=1)

Blocking  
Assn.

```
reg a, b, c;  
initial begin  
    #50;  
    b = a;  
    c = b;  
end
```


Cycle	a	b	c
0	0	1	
50	0	0	0



Non-blocking  
Assn.

```
reg a, b, c;  
initial begin  
    #50;  
    b <= a;  
    c <= b;  
end
```

Cycle	a	b	c
0	0	1	
50	0	0	1



# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- **Verilog Simulation**

# Delay

- **Purpose of Delay Assignment**

- To Imposing delay during simulation
  - clock signal generation, stimulus signal input
- Realistic hardware delay modeling
  - wire RC timing delay, gate delay
- In this course, use delay only at testbench for sim.

- **Accumulation of delay**

- Delays are accumulated in a procedure

```
initial begin
    #50 clk = 0;
    #50 x = 1;
end
```

=

```
initial #50 clk = 0;
initial #100 x = 1;
```

# Event

- Purpose of Event Assignment

```
module dummy (input a,  
              output b);  
  reg b;  
  event e;  
  initial begin  
    #50;  
    -> e;  
  end
```

*After 50 delay units,  
e is executed*

```
    always @e begin  
      b <= 1;  
    end  
endmodule
```

*Every time the event e happens  
procedure is always executed*

- Assigning executing condition to peocedures

# Cases of Event

- How to Assign Events

- Data change as event

```
reg a;  
always @ (a) begin  
    ...  
end
```

- The moment of value change as event

```
reg a;  
always @ (posedge a) begin // when a 0 → 1  
always @ (negedge a) begin // when a 1 → 0
```

- Logically combining events

```
always @ (posedge clk or negedge rst_n)  
    // very typical structure in sequential logic
```

# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- **Verilog Simulation**

# Flow Control Statements: If

- If Statement

- Conditional execution of statement
- Trinomial operator in C

```
initial begin
    if (a == 5) begin
        b <= 15;
    end
    else begin
        b <= 25;
    end
end
```

==

```
wire c = (a == 5) ? 15 : 25;
initial begin
    b <= c;
end
```



# Flow Control Statements: Case

- **Case Statement**

- Multi-conditional execution of statement

```
initial begin
  if (a == 5) begin
    b <= 15;
  end
  else begin
    b <= 25;
  end
end
```

=

```
initial begin
  case (a)
    5 : b <= 15;
    default : b <= 25;
  endcase
end
```

# Flow Control Statements: Loop

- **Loop Statement: Usually used in testbench**
  - Repeat: execute statement for finite times

```
initial begin
```

```
    repeat (4) c = c + 1;
```

```
end
```

=

```
initial begin
```

```
    c = c + 1;
```

```
    c = c + 1;
```

```
    c = c + 1;
```

```
    c = c + 1;
```

```
end
```

```
initial begin
```

```
    forever #5 c = c + 1;
```

```
end
```

=

```
initial begin
```

```
    #5 c = c + 1;
```

```
    #5 c = c + 1;
```

```
    #5 c = c + 1;
```

```
    #5 c = c + 1;
```

```
End// infinitely repeat
```

# Flow Control Statements: Loop

- **Conditional Loop: `while`, `for`**
  - Used like in C
  - Generally not synthesizable
  - Usually only used in testbench

```
reg c;  
initial begin  
    while (c < 10)  
        c = c + 1;  
end
```

```
reg c;  
initial begin  
    for (c = 0; c < 10; c = c + 1)  
        // Statement  
end
```

# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- Verilog Simulation


# Concept of FSM

- **Finite State Machine**

- Deterministic Finite Automata
- A machine with only deterministic finite states
- Mealy machine vs Moore machine


- **Moore Machine**

 - Output is determined
  - by current state
- Next state is determined
  - by current state & input



- **Mealy Machine**

 - Output is determined
  - by current state & input
- Next state is determined
  - by current state & input



# Moore Machine Example

```
module MOORE (  
    input    wire    CLK,  
    input    wire    RST,  
    input    wire    IN,  
    output   reg     OUT  
);  
localparam  S_A = 2'b00;    // state A  
localparam  S_B = 2'b01;    // state B  
localparam  S_C = 2'b10;    // state C  
  
reg  [1:0]  CurState;    // Current state  
reg  [1:0]  NextState;   // Next state  
  
always @ (posedge CLK)  
    if (RST)  
        CurState = S_A;  
    else  
        CurState = NextState;  
  
    ...
```

Parameter definition which can  
not be changed from outside

```
    ...  
  
always @ *  
    case ({CurState, IN})  
        {S_A, 1'b0} : NextState = S_B;  
        {S_A, 1'b1} : NextState = S_C;  
        {S_B, 1'b0} : NextState = S_B;  
        {S_B, 1'b1} : NextState = S_C;  
        {S_C, 1'b0} : NextState = S_B;  
        {S_C, 1'b1} : NextState = S_C;  
        default: NextState = S_A;  
    endcase  
  
always @ *  
    case (CurState)  
        S_A : OUT = 1'b0;  
        S_B : OUT = 1'b0;  
        S_C : OUT = 1'b1;  
        default: OUT = 1'b0;  
    endcase  
  
endmodule
```

# Mealy Machine Example

```
module MEALY (  
    input    wire    CLK,  
    input    wire    RST,  
    input    wire    IN,  
    output   reg     OUT  
);  
localparam  S_A = 2'b00; // state A  
localparam  S_B = 2'b01; // state B  
localparam  S_C = 2'b10; // state C  
  
reg  [1:0]  CurState; // Current state  
reg  [1:0]  NextState; // Next state  
  
always @ (posedge CLK)  
    if (RST)  
        CurState = S_A;  
    else  
        CurState = NextState;  
  
    ...
```

```
    ...  
  
    always @ *  
        case ({CurState, IN})  
            {S_A, 1'b0} :  
                {NextState, OUT} = {S_B, 1'b0};  
            {S_A, 1'b1} :  
                {NextState, OUT} = {S_C, 1'b0};  
            {S_B, 1'b0} :  
                {NextState, OUT} = {S_B, 1'b0};  
            {S_B, 1'b1} :  
                {NextState, OUT} = {S_C, 1'b1};  
            {S_C, 1'b0} :  
                {NextState, OUT} = {S_B, 1'b1};  
            {S_C, 1'b1} :  
                {NextState, OUT} = {S_C, 1'b0};  
            default:  
                {NextState, OUT} = {S_A, 1'b0};  
        endcase  
  
endmodule
```

# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- **Verilog Syntax**
  - Module Body
  - Assignments
  - Delay & Event
  - Flow Control
  - Design Method: FSM
  - More on Verilog Syntax
- Verilog Simulation



# More on Verilog Syntax

---

- **Comment**

- `//` or `/* ... */` → the same with C language

- **Constant**

- Format: `<the num. of bits>'<number system><value>`
- `<number system>`
  - h(hexadecimal), d(decimal), o(octal), b(binary)
- `<value>`
  - 0~9, A~F, X(undefined), Z(High Impedance)
- `_`(underbar): for better visibility of long digit values
- Just number can be used for decimal numbers
  - ex) 8'b0100\_1111 (8-bit binary 01001111)  
16'hAF (16-bit hexadecimal AF)

# More on Verilog Syntax

- **Operators**

- Similar to C language operators except for ++ and --
- Monomial / binomial logical operators:  
and(&), nand(~&), or(|), nor(~|), xor(^), xnor(~^), not(~)
- Equality operators  
a==b, a!=b → return x if a or b is x or z  
a===b, a!==b → comparison including x and z

- **Array and Vectors**

```
reg [31:0] memory [0:511];           // 32-bit memory w/ 512 elem.  
reg          regA    [3:0][0:511];   // 2D array of 1-bit reg  
wire [7:0] bus_array [0:511];        // 8-bit bus array of size 12
```

# Reference

---

- Verilog Study Webpages
  - Verilog Tutorial & Examples  
<http://www.asic-world.com/verilog/index.html>
  - Verilog Syntax: Compact Summary  
<https://www.csee.umbc.edu/portal/help/VHDL/verilog/summary.html>

# Outline


---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- Verilog Syntax
- **Verilog Simulation**
  - Verilog RTL Simulation
  - Simulation using ModelSim

# Verilog RTL Simulation

- Procedures of Verilog Simulation

- Similar to C programming

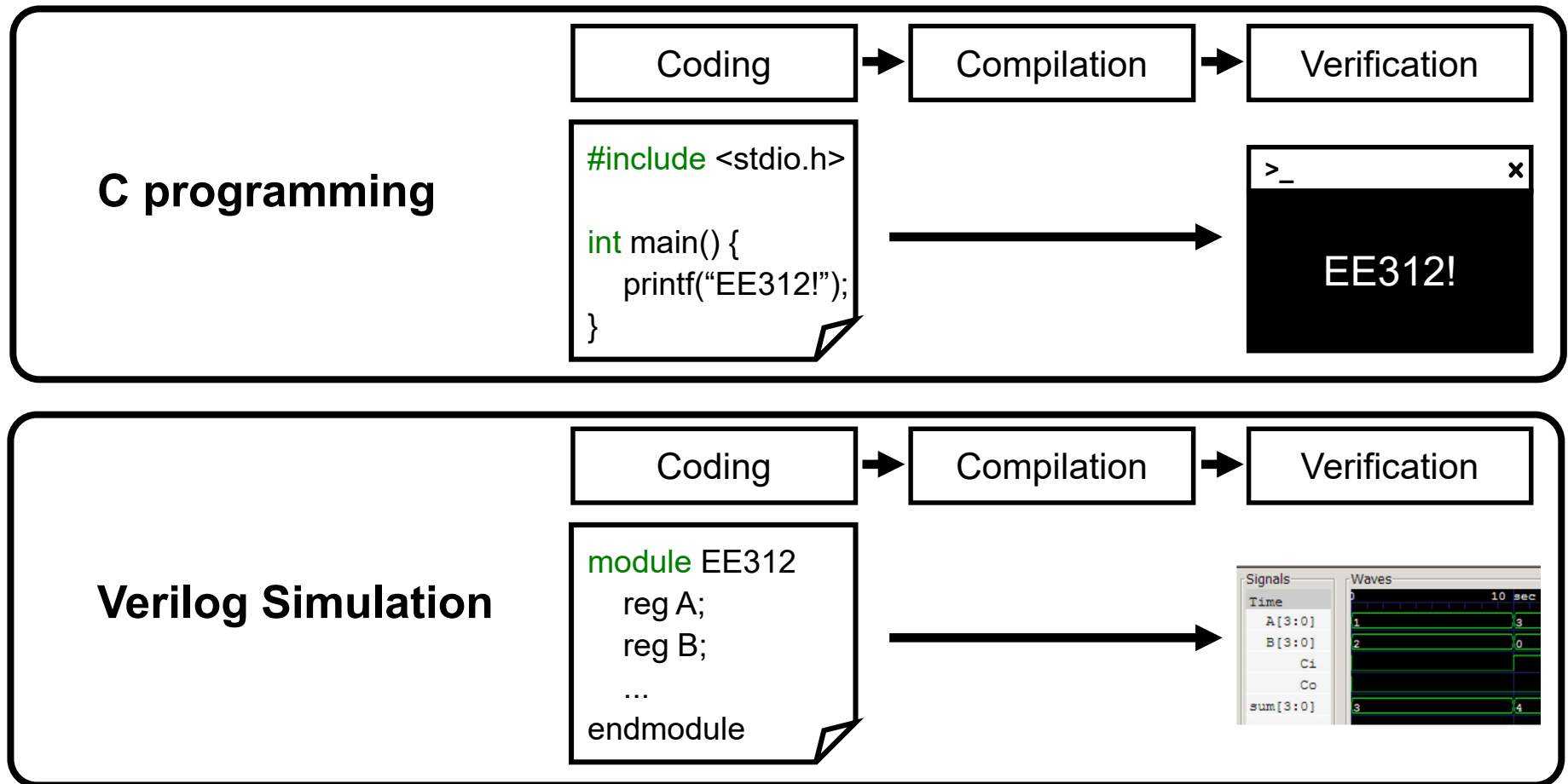


# Testbench for Test Designed Module

- **Testbench**

- Test signal generation and output data recording with instantiation of the designed module
- Test signal (stimulus) generation as input to DUT

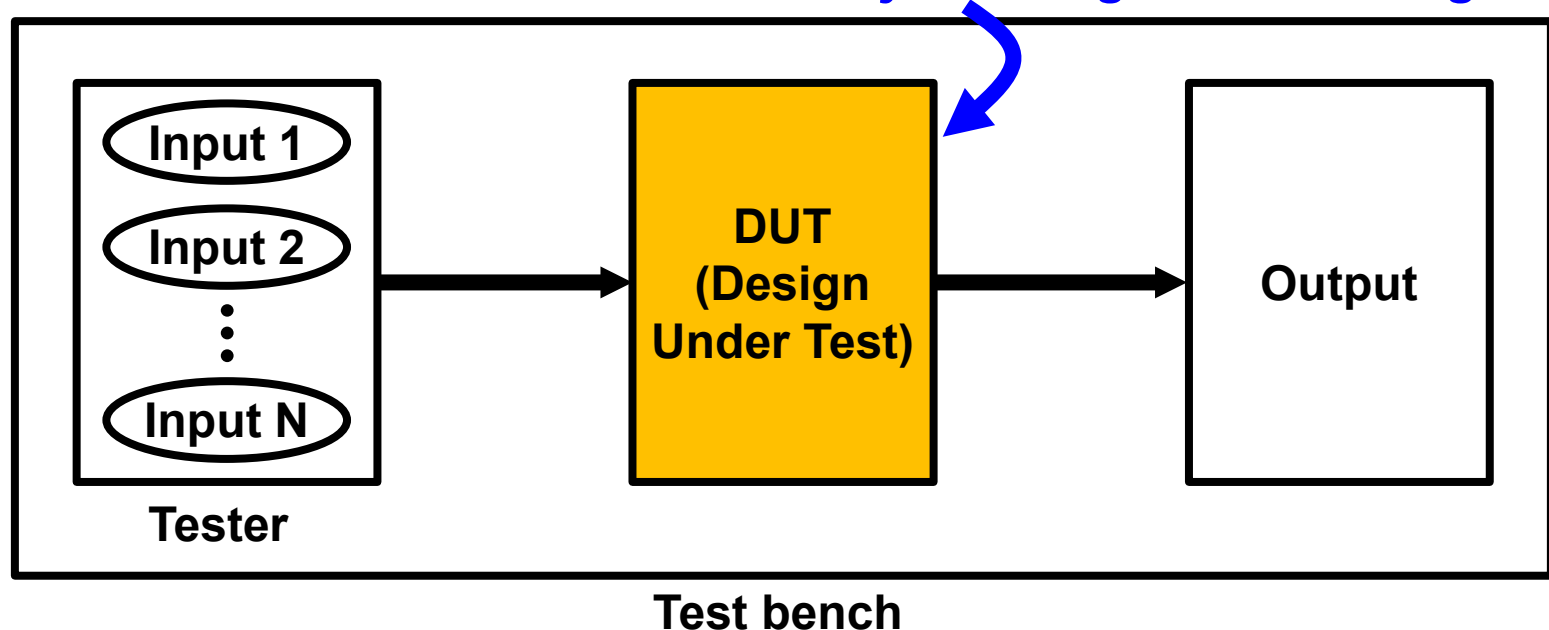*The Module Instantiation you designed in Verilog*



# Outline

---

- Lab Class Operating Plan
- Verilog HDL: Introduction
- Verilog Syntax
- **Verilog Simulation**
  - Verilog RTL Simulation
  - Simulation using ModelSim

# ModelSim Guide

---

- Please refer to
  - “[EE312]ModelSim\_guide.pdf”